



7. Is flipping a switch the only way to create an open circuit? Explain.

### **Solving Problems**

1. Draw a circuit diagram of a circuit with a battery, three wires, a light bulb and a switch.